


Diode Problem 3.42

Mandy Liu

The Problem

3.42 Consider the circuit in Fig. 3.10 with $V_{DD} = 3$ V and $R = 3$ k Ω .

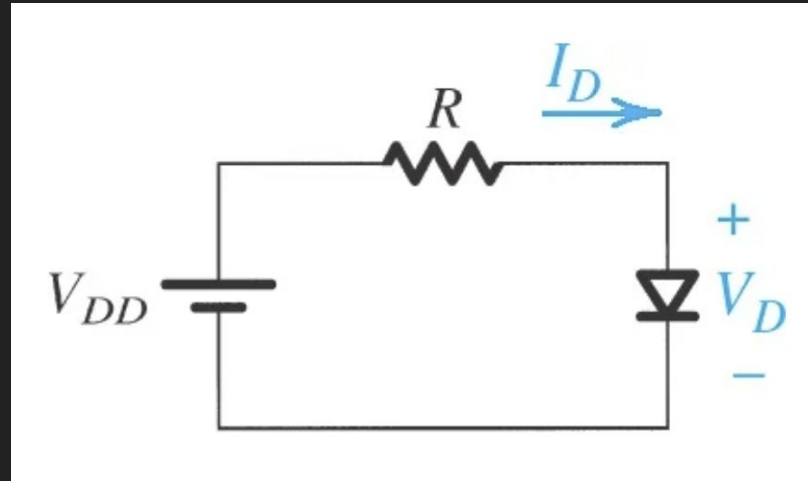- (a) Find the current using a constant-voltage-drop model.
- (b) What value of I_S is required to make this solution exact?
- (c) Approximately how much will the current change from this value if I_S increases by a factor of 100?



The Problem

What's given:

- $V_{DD} = 3V$
- $R = 3 \text{ k Ohm}$

What needs to be found:


- Current using the constant voltage drop model
- Value of I_s
- Current change if the value I_s increases by factor of 100

Part A: Finding the Current

Diode is in the forward direction and have a voltage drop of 0.7V across.

Apply simple KVL

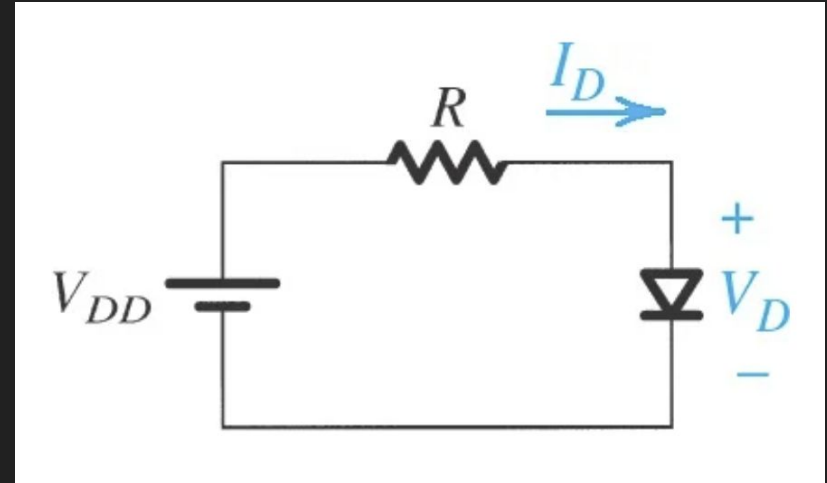$V_{DD} = 3V$ $V_D = 0.7V$ $R = 3000 \text{ ohms}$



$$I_D = \frac{V_{DD} - V_D}{R}$$

$$I_D = \frac{3V - 0.7V}{3000\Omega} = \boxed{0.767 \times 10^{-3}A}$$

Part B: Finding the value of I_s

Diode is in the forward direction and have a voltage drop of 0.7V across.

Use the forward-biased diode current equation (in blue)

$$I_D = 0.767\text{mA} \quad V_D = 0.7\text{V} \quad V_T = 25.9\text{mA}$$

$$I_s = \frac{I_D}{e^{V_D/V_T}}$$

$$I_s = \frac{0.767 \times 10^{-3} \text{A}}{e^{0.7\text{V} / 25.9 \times 10^{-3} \text{A}}} = \boxed{1.40 \times 10^{-15} \text{A}}$$

Part C: Current change

Determine the value for I_s' when I_s is increased by a factor of 100

Multiply I_s by 100

$$I_s = 1.40 \times 10^{-15} \text{ A}$$

$$I_s' = 100 \times I_s$$

$$I_s' = 100 \times (1.40 \times 10^{-15}) = \boxed{1.40 \times 10^{-13} \text{ A}}$$

Part C: Current change

Determine the value for I_D when I_s is increased by a factor of 100

Use the forward-biased diode current equation (in blue)

$$I_s' = 1.40 \times 10^{-13} \text{ A} \quad V_D = 0.7 \text{ V} \quad V_T = 25.9 \times 10^{-3} \text{ V}$$

$$I_D' = I_s' e^{V_D/V_T}$$

$$I_D' = 1.40 \times 10^{-13} e^{0.7 \text{ V} / 25.9 \times 10^{-3} \text{ V}} = \boxed{76.5 \times 10^{-3} \text{ A}}$$

Part C: Current change

Determine the change between I_D' and I_D

Subtract I_D' by I_D

$$I_D' = 76.5 \text{ mA} \quad I_D = 0.767 \text{ mA}$$

$$\Delta I = I_D' - I_D$$

$$\Delta I = 76.5 \times 10^{-3} \text{ A} - 0.767 \times 10^{-3} = \boxed{75.7 \times 10^{-3} \text{ A}}$$